

## Diode Application

① Limiter Clipping


2 Clamping

③ Voltage doubler

① \* Limiter-Clipping

①  $V > 0 \rightarrow$  diode is on  $\rightarrow V_{out} = I \cdot R$

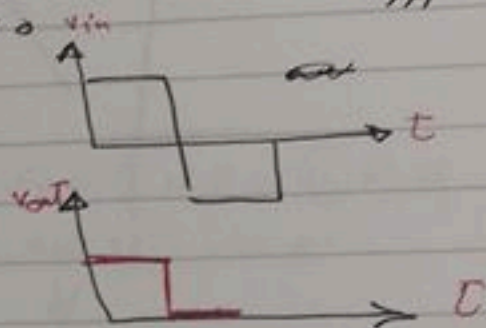$V < 0$  diode is off  $\rightarrow V_{out} = 0$




① +ve half wave

$$V_o = 0$$

② -ve half wave


$$V_o = V_{in}$$

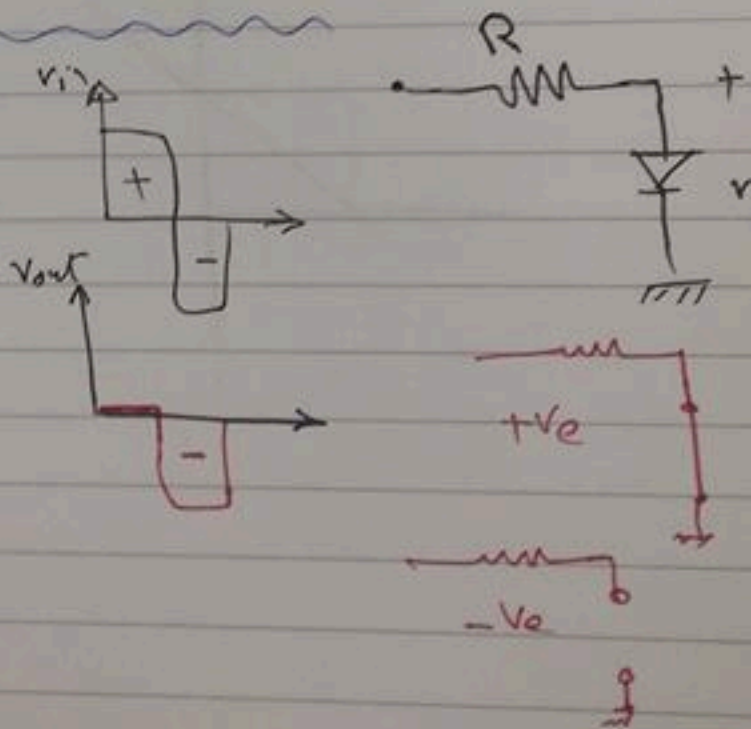
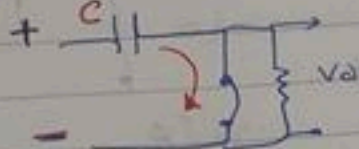
## ② Clamping :-


Clamping يعني في مكنة في الدارة.

①  $V_{in} > 0$  : Diode is on  $\rightarrow$  S.C



$$\therefore V_o = 0$$

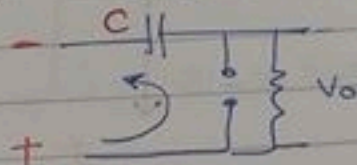②  $V_{in} < 0$  : Diode is off  $\rightarrow$  o.c



$$\therefore V_o = -2V_{in}$$

\* في حالة forward يكون  $V = V_{in}$  بسبب استمرارية التيار

في حالة Revers. يكون الجهد على التوافيق

$$2V_{in} = V_c + V_{in} =$$

$$f = 1 \text{ kHz} = 1000 \text{ Hz}$$

$$T = \frac{1}{1000} = 1 \text{ ms}$$







① from  $T=0 \rightarrow T_1$  Diode is S.C

$$T_1 = \frac{T}{2} = 0.5 \text{ ms}$$

$$V_{out} = 0$$

② from  $T_1 \rightarrow T_2$  Diode is o.c


$$V_{out} = -15$$

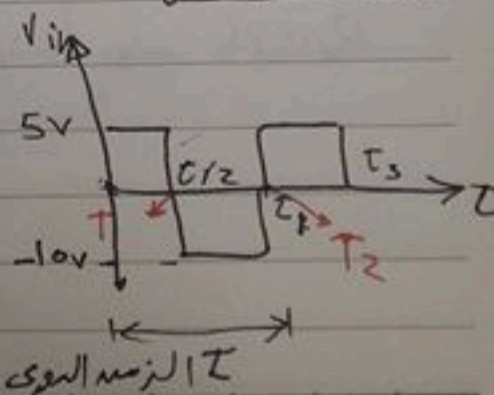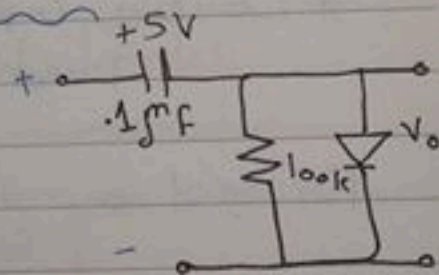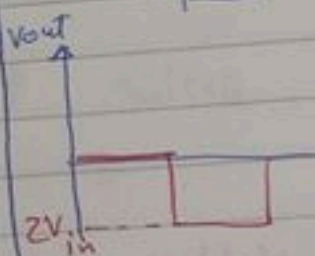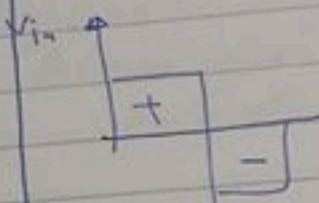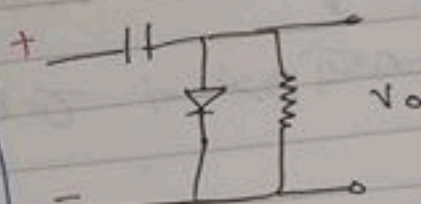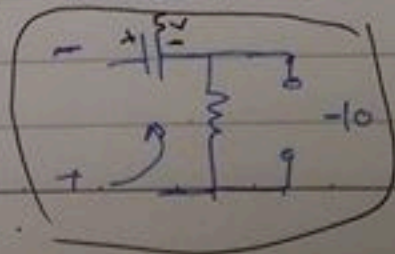




$$\tau = RC = .1 \times 10^{-6} \times 100 \times 10^3$$

$\tau = 10 \text{ m.s}$

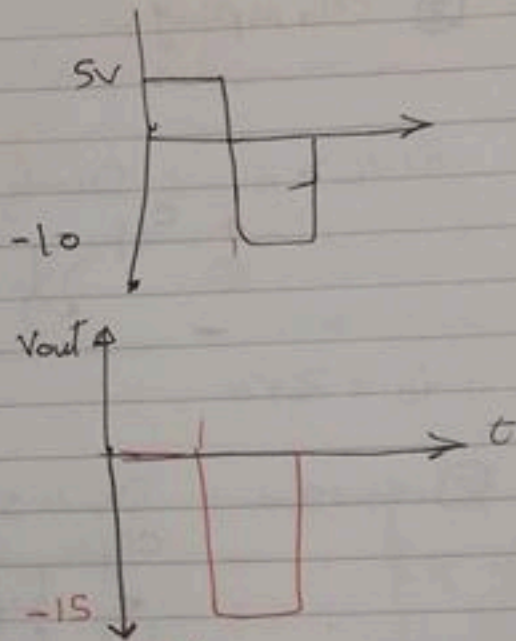

(3) Voltage doubler

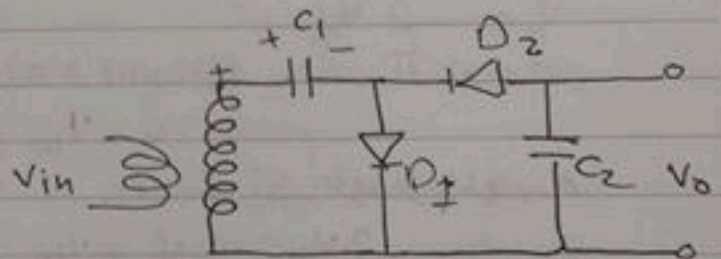

\* Double input with  $(-V_e)$  sign  
Inverted wave.

Forward  $\Rightarrow V_{out} = 2 V_{in}$

Reverse  $\Rightarrow V_{out} = -2 V_{in}$

# transistor

1\* Switch

off → on  
"Saturation"

2\* Amplifier  
"Active Region"

مکبر





Playing → Biasing → ↑↑ Voltage

Sleep → " ↓↓


B as to Base

transistor.



emitter E ← n | p | n → C Collector

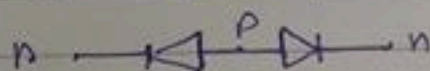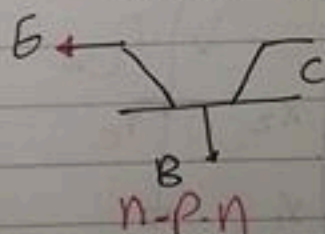

Back to Back Diodes

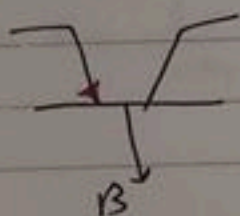

P-n-p

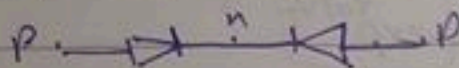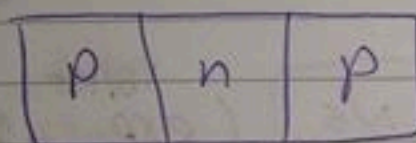




# Active transistor

## Amplifier


الترانزستور كـ مضخم

علاقة الترانزستور مع  
التيار  $I_E$   $I_B$   $I_C$

$I_E = I_B + I_C$

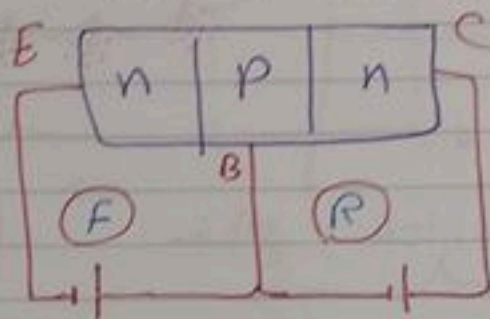


$$100 A = I_{Base}$$

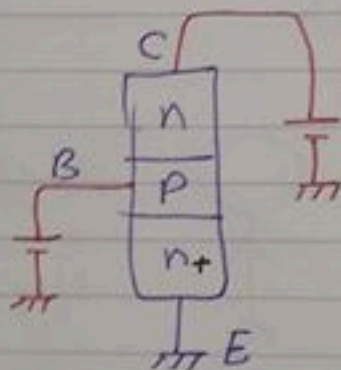
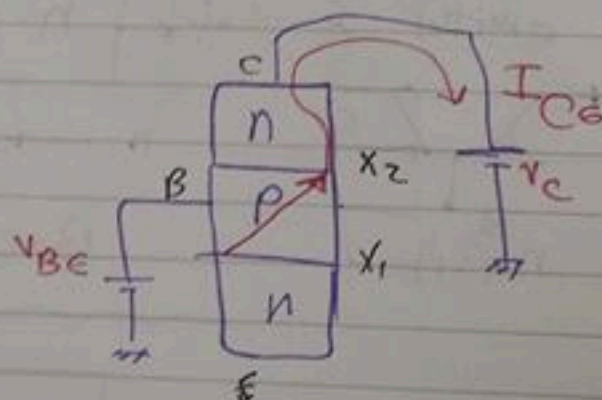
## \* Collector Current

$$\Delta n(x_1) \propto \left( \exp^{\frac{V_{BE}}{kT}} - 1 \right)$$



$$\Delta n(x_1) = \frac{N_E}{\exp^{\frac{V_{BE}}{kT}}} \left( \exp^{\frac{V_{BE}}{kT}} - 1 \right)$$

$N_E \rightarrow$  تركيز الحاملات  
في الـ emitter

$$V_o = V_T \ln \left( \frac{N_A N_D}{n_i^2} \right) \leftarrow \text{Diode}$$

$$\frac{V_o/V_T}{e} = \frac{N_A N_D}{n_i^2}$$

transistor

بالعمود

$\Delta n(x_1)$  العنصر

$$\therefore \Delta n(x_1) = \frac{n_i^2}{N_B} \left( \exp^{V_{BE}/V_T} - 1 \right)$$

$$J_n = q D_n \frac{dn}{dx} = q D_n \left( \frac{0 - \Delta n(x_1)}{w_B} \right) \rightarrow \text{Base } \Delta n \text{ و } w_B$$



التيار العنصر

$$I_C = \frac{A_E * q D_n n_i^2}{N_B w_B} \left( \exp^{V_{BE}/V_T} - 1 \right)$$

$\downarrow$   
 $I_S$

$$\therefore I_C = I_S \left( \exp \left( \frac{V_{BE}}{V_T} \right) - 1 \right)$$

$\downarrow$   
التيار

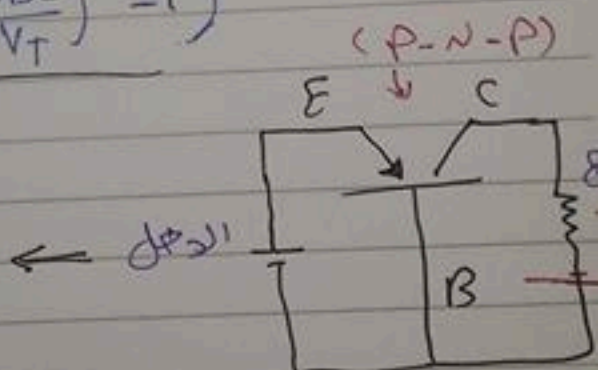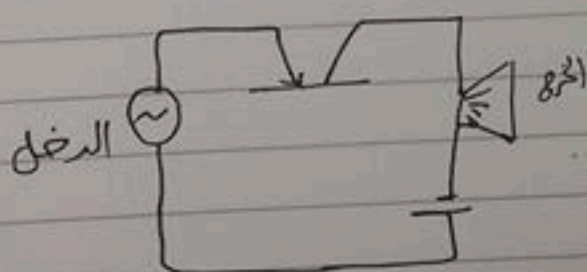

$$10 \text{ mV} \quad 1 \text{ V}$$

$$1000 \times = \frac{1 \text{ V}}{10 \text{ mV}} = \text{نسبة التكبير}$$



$$V_0 = V_T \ln \left( \frac{N_A N_D}{n_i^2} \right) \leftarrow \text{Diode}$$

$$\frac{V_0/V_T}{e} = \frac{N_B N_B}{n_i^2} \leftarrow \text{Transistor}$$

⇒

معنوسه  
 $\Delta n(x_1)$  ابلزل

$$\therefore \Delta n(x_1) = \frac{n_i^2}{N_B} (\exp^{V_{BE}/V_T} - 1)$$

$$J_n = q D_n \frac{dn}{dx} = q D_n \left( \frac{0 - \Delta n(x_1)}{w_B} \right) \leftarrow \text{Base } n \text{ eff}$$



جمل ابلزل

$$I_C = \frac{A_G \times q D_n n_i^2}{N_B w_B} (\exp^{V_{BE}/V_T} - 1)$$

$\downarrow$   
 $I_S$

$$\therefore I_C = I_S \left( \exp \left( \frac{V_{BE}}{V_T} \right) - 1 \right)$$

$\downarrow$   
جمل

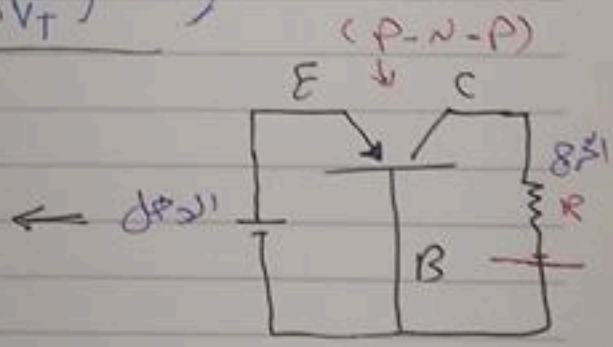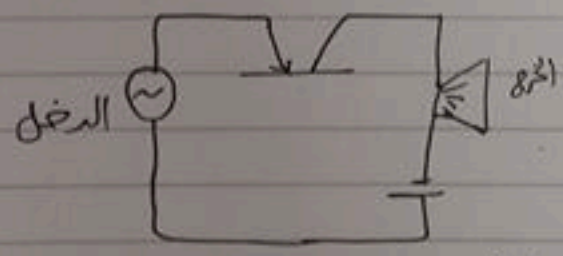

$$\frac{10 \text{ mV}}{1000} = \frac{1 \text{ V}}{10 \text{ mV}} = \text{نسبة التكبير}$$